

Report HW 3 ECE-111

Name: Jasper Huang

PID: A17796149

Homework 3a (Johnson Counter)

1. SystemVerilog design code

a. johnson_counter


```
module johnson_counter (  
    input logic clk, clear, preset,  
    input logic[3:0] load_cnt,  
    output logic[3:0] count  
);  
    always @(posedge clk or negedge clear) begin  
        // Student to add code for Johnson Counter  
        if (!clear) begin  
            count = 4'b0000;  
        end else if (!preset) begin  
            count = load_cnt;  
        end else begin  
            count = {~count[0], count[3:1]};  
        end  
    end  
endmodule: johnson_counter
```

2. Synthesis Resource usage and schematic generated from RTL netlist viewer


a. Resource Usage

Analysis & Synthesis Resource Usage Summary		
<<Filter>>		
	Resource	Usage
1	Estimate of Logic utilization (ALMs needed)	2
2		
3	▼ Combinational ALUT usage for logic	4
1	-- 7 input functions	0
2	-- 6 input functions	0
3	-- 5 input functions	0
4	-- 4 input functions	0
5	-- <=3 input functions	4
4		
5	Dedicated logic registers	4
6		
7	I/O pins	11
8		
9	Total DSP Blocks	0
10		
11	Maximum fan-out node	preset~input
12	Maximum fan-out	4
13	Total fan-out	39
14	Average fan-out	1.30

b. RTL netlist viewer

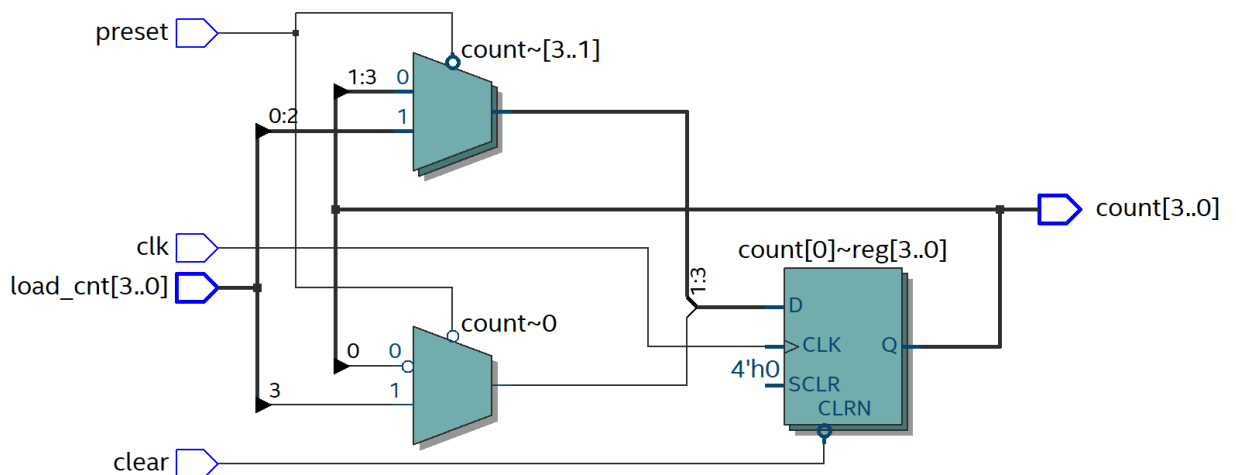

4. Post-Mapping schematic

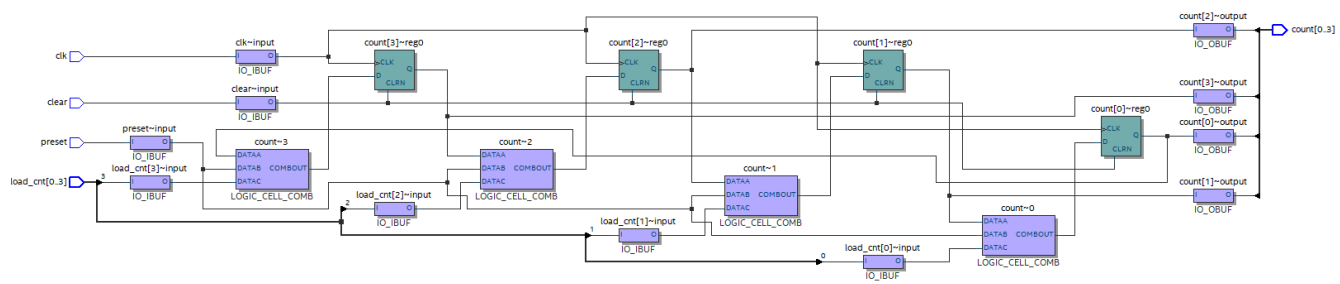

Homework 3b (Universal Shift Register)

1. SystemVerilog code snapshot

a. universal_shift_register (student fill part)


```
// student to fill code for SIPO-L, SIPO-R, PISO-L, PISO-R, SISO-L, SISO-R operation mode of shift register
// Note : Use non-blocking assignment statements within case item expressions
3'b001 : begin
    shift_reg <= {shift_reg[2:0], sin};
    sout <= 1'b0;
end
3'b010 : begin
    shift_reg <= {sin, shift_reg[3:1]};
    sout <= 1'b0;
end
3'b011 : begin
    shift_reg <= {shift_reg[2:0], 1'b0};
    sout <= shift_reg[3];
end
3'b100 : begin
    shift_reg <= {1'b0, shift_reg[3:1]};
    sout <= shift_reg[0];
end
3'b101 : begin
    shift_reg <= {shift_reg[2:0], sin};
    sout <= shift_reg[3];
end
3'b110 : begin
    shift_reg <= {sin, shift_reg[3:1]};
    sout <= shift_reg[0];
end
default : begin
    shift_reg <= 4'b0000;
    sout <= 1'b0;
end
```

2. Synthesis Resource usage and schematic generated from RTL netlist viewer


a. Synthesis Resource usage

Analysis & Synthesis Resource Usage Summary		
<<Filter>>		
	Resource	Usage
1	Estimate of Logic utilization (ALMs needed)	9
2		
3	▼ Combinational ALUT usage for logic	11
1	-- 7 input functions	3
2	-- 6 input functions	4
3	-- 5 input functions	2
4	-- 4 input functions	1
5	-- <=3 input functions	1
4		
5	Dedicated logic registers	5
6		
7	I/O pins	16
8		
9	Total DSP Blocks	0
10		
11	Maximum fan-out node	reset~input
12	Maximum fan-out	9
13	Total fan-out	97
14	Average fan-out	2.02

b. RTL netlist viewer

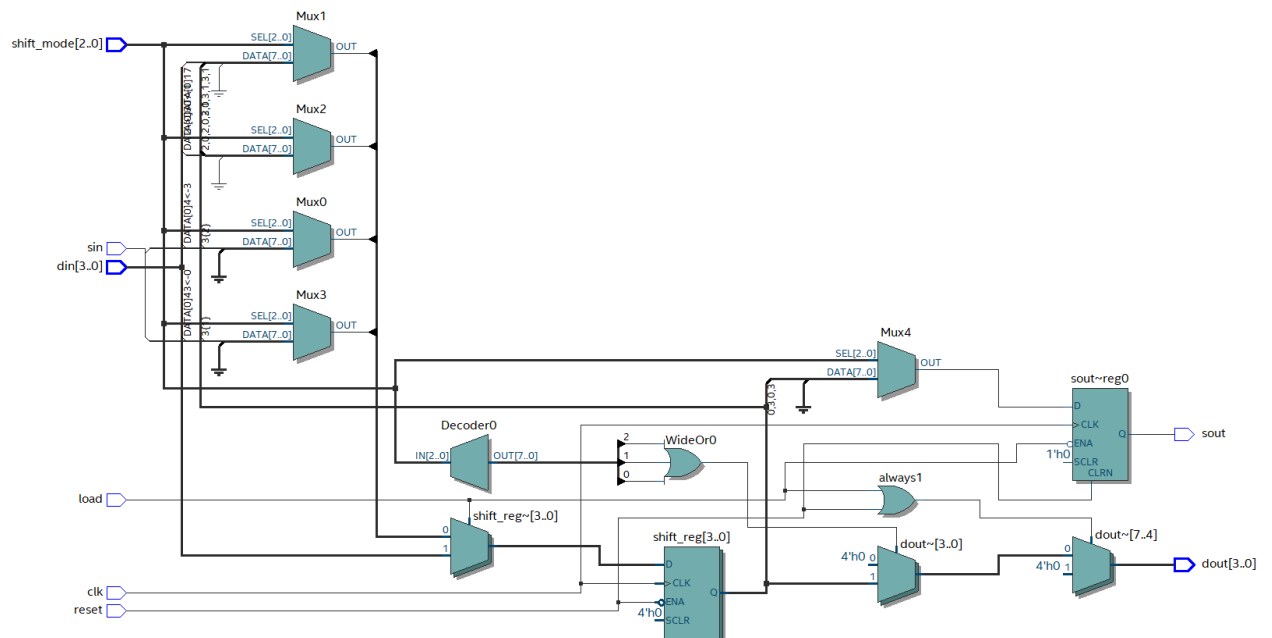

 3. Simulation snapshot and explain simulation result



For different shift modes, the operations perform as expected, with each of the following:

- 000: PIPO, which gives a dout 1001, output of din = 1001
- 001: SIPO-L, which gives a dout of 1101, output of sin = 1,1,0,1 from left to right
- 010: SIPO-R, which gives dout of 1110, output of sin = 0,1,1,1 from right to left
- 011: PISO-L, which gives a sout of 1,1,0,1, output of din = 1101 from left to right
- 100: PISO-R, which gives a sout of 0,0,0,1, output of din = 1000 from right to left
- 101: SISO-L, which gives a sout of 1,0,1,0, output of sin = 1,0,1,0 with a different order in shift reg
- 110: SISO-R, which gives a sout of 1,1,0,1, output of sin = 1,1,0,1 with a different order in shift reg

All waveform matches the expected calculation (including serial and parallel out) for each operation.

4. Post-Mapping schematic

