

# Report HW 0 ECE-111

Name: Jasper Huang

PID: A17796149

## 2-to-4 decoder

### 1. Behavioral level


#### a. SystemVerilog Code

```
// 2to4 Decoder behavioral level code
module decoder_2to4_behavioral(
    input  logic[1:0] sel,
    output logic[3:0] out
);
    always @(sel or out)
    begin
        case (sel)
            2'b00 : out = 4'b0001;


            // Student to add remainder of the code
            2'b01 : out = 4'b0010;
            2'b10 : out = 4'b0100;
            2'b11 : out = 4'b1000;
            default: out = 4'b0000;

        endcase
    end
endmodule
```

#### b. RTL Schematic

 

### c. Post mapping schematic

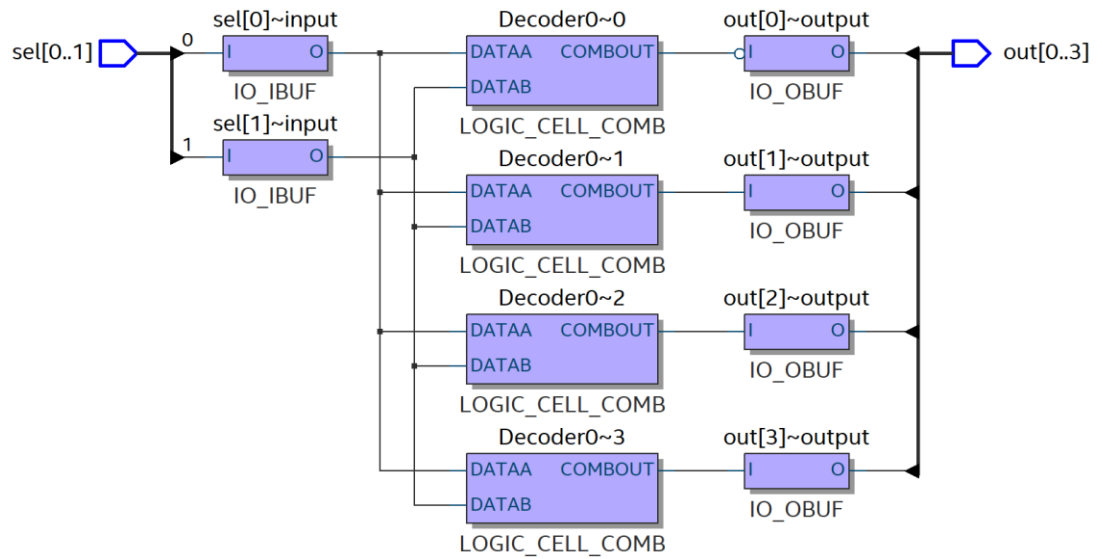

### d. Resource Usage

Analysis & Synthesis Resource Usage Summary		
<<Filter>>		
	Resource	Usage
1	Estimate of Logic utilization (ALMs needed)	2
2		
3	✓ Combinational ALUT usage for logic	4
1	-- 7 input functions	0
2	-- 6 input functions	0
3	-- 5 input functions	0
4	-- 4 input functions	0
5	-- <=3 input functions	4
4		
5	Dedicated logic registers	0
6		
7	I/O pins	6
8		
9	Total DSP Blocks	0
10		
11	Maximum fan-out node	<code>sel[0]~input</code>
12	Maximum fan-out	4
13	Total fan-out	18
14	Average fan-out	1.13


**Number of ALUT:** 4 (6 I/O pins)

4 ALUTs each for the output, which there are 4 outputs

**Number of Functions:** 4 (2 input function)

Require 4 2-input function for each output (2 input for sel\_0 sel\_1)

**e. Modelsim simulation results**

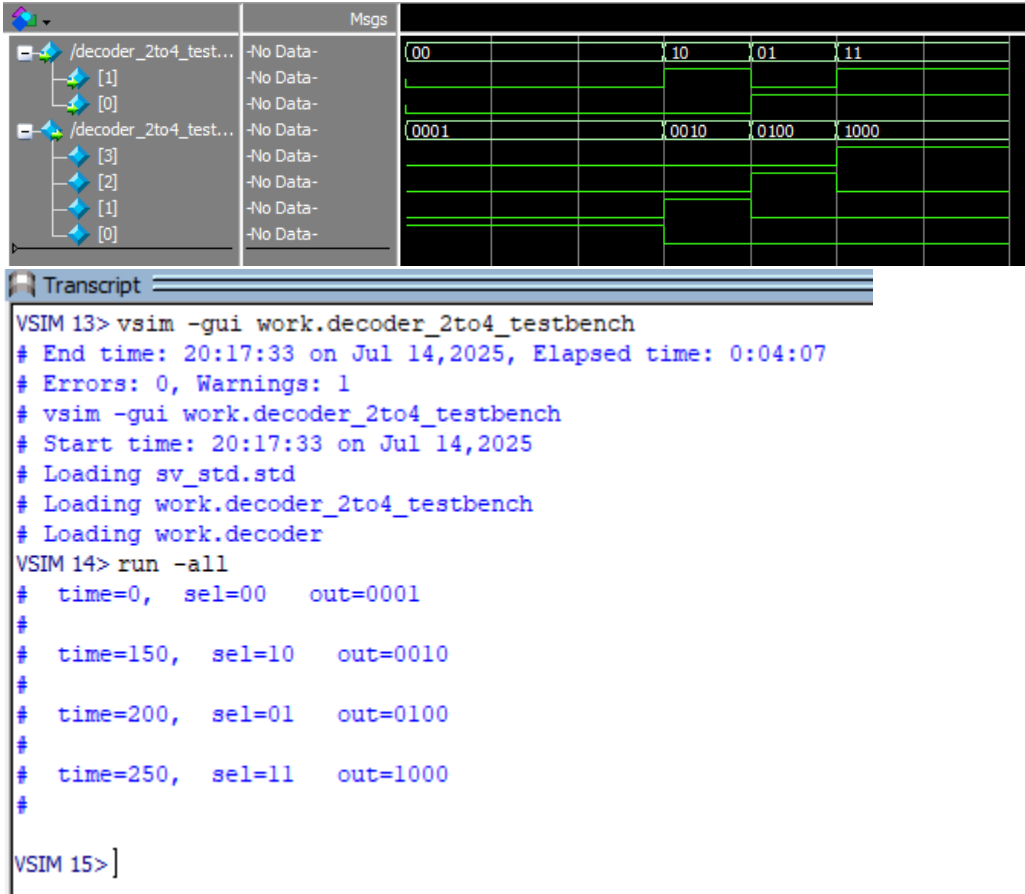


The decoder transform the 2 bit input into 1 in the corresponding position.

**2. Dataflow level**


**a. SystemVerilog Code**

```
// 2to4 Decoder dataflow level code
module decoder_2to4_dataflow(
  input  logic[1:0] sel,
  output logic[3:0] out
);
  assign out[0] = (!sel[0]) && (!sel[1]);
  // Student to add remainder of the assign statements
  assign out[1] = (!sel[1]) & sel[0];
  assign out[2] = sel[1] & (!sel[0]);
  assign out[3] = sel[1] & sel[0];
endmodule
```

b. RTL schematic

 

c. Post mapping schematic

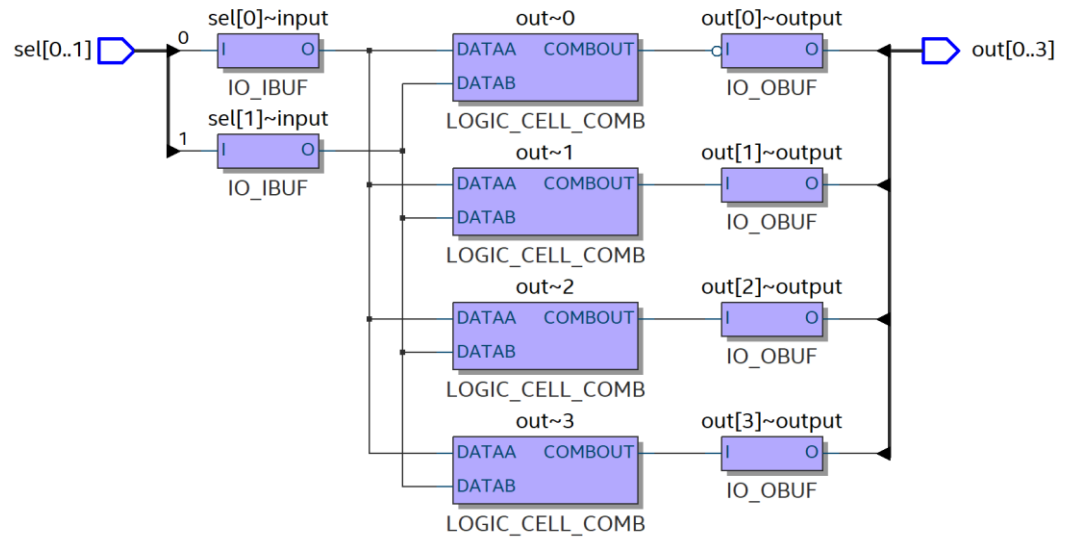

#### d. Resource usage

Analysis & Synthesis Resource Usage Summary		
<<Filter>>		
	Resource	Usage
1	Estimate of Logic utilization (ALMs needed)	2
2		
3	Combinational ALUT usage for logic	4
1	-- 7 input functions	0
2	-- 6 input functions	0
3	-- 5 input functions	0
4	-- 4 input functions	0
5	-- <=3 input functions	4
4		
5	Dedicated logic registers	0
6		
7	I/O pins	6
8		
9	Total DSP Blocks	0
10		
11	Maximum fan-out node	<code>sel[0]~input</code>
12	Maximum fan-out	4
13	Total fan-out	18
14	Average fan-out	1.13


#### e. Modelsim simulation result (same as behavioral level simulation result)

### 3. Gatelevel


a. SystemVerilog Code

```
// 2to4 Decoder gatelevel code
module decoder_2to4_gate(
  input  logic[1:0] sel,
  output logic[3:0] out
);
  wire w0, w1;
  not i0(w0, sel[0]);
  not i1(w1, sel[1]);
  and g0(out[0], w1, w0);
  and g1(out[1], sel[1], w0);
  and g2(out[2], w1, sel[0]);
  and g3(out[3], sel[1], sel[0]);
endmodule
```

b. RTL schematic

 

c. Post mapping schematic

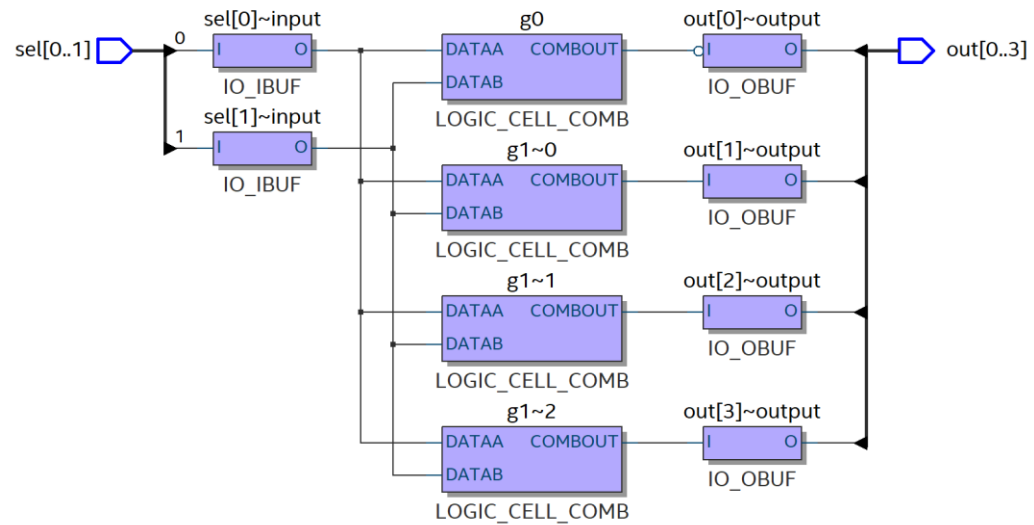

#### d. Resource usage


Analysis & Synthesis Resource Usage Summary		
<<Filter>>		
	Resource	Usage
1	Estimate of Logic utilization (ALMs needed)	2
2		
3	Combinational ALUT usage for logic	4
1	-- 7 input functions	0
2	-- 6 input functions	0
3	-- 5 input functions	0
4	-- 4 input functions	0
5	-- <=3 input functions	4
4		
5	Dedicated logic registers	0
6		
7	I/O pins	6
8		
9	Total DSP Blocks	0
10		
11	Maximum fan-out node	sel[0]~input
12	Maximum fan-out	4
13	Total fan-out	18
14	Average fan-out	1.13

#### e. Modelsim simulation result (same as behavioral level simulation result)


## 2-to-1 Mux

### 1. Behavioral level

#### a. RTL schematic

 

#### b. Post mapping schematic

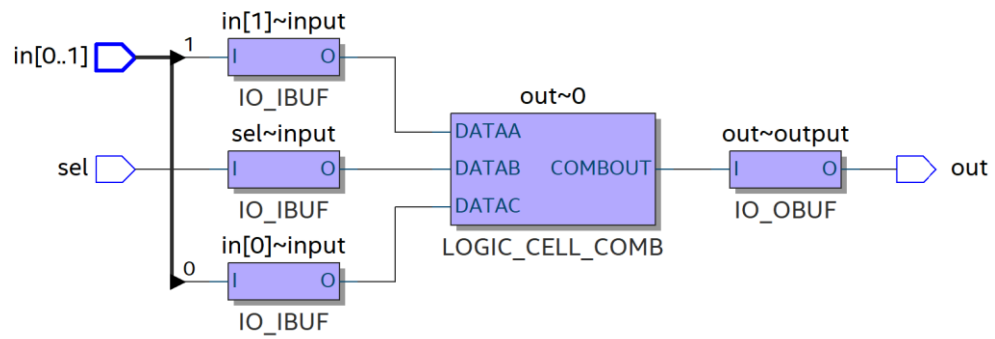

#### c. Resource usage



## Analysis & Synthesis Resource Usage Summary

<<Filter>>

	Resource	Usage
1	Estimate of Logic utilization (ALMs needed)	1
2		
3	▼ Combinational ALUT usage for logic	1
1	-- 7 input functions	0
2	-- 6 input functions	0
3	-- 5 input functions	0
4	-- 4 input functions	0
5	-- <=3 input functions	1
4		
5	Dedicated logic registers	0
6		
7	I/O pins	4
8		
9	Total DSP Blocks	0
10		
11	Maximum fan-out node	out~0
12	Maximum fan-out	1
13	Total fan-out	8
14	Average fan-out	0.89


**Number of ALUT:** 1 (4 I/O pins)

2:1 MUX design need only one ALUT for the single output

**Number of Functions:** 1 (3 input function)

Require 1 3-input function for the single output, with 3 input in\_0, in\_1, and sel

### d. Modelsim simulation result

 

```


Transcript
# Start time: 20:46:27 On Oct 14, 2025
# Loading sv_std.std
# Loading work.mux_2x1_testbench
# Loading work.mux_2x1
add wave -position end sim:/mux_2x1_testbench/tb_in
add wave -position end sim:/mux_2x1_testbench/tb_sel
add wave -position end sim:/mux_2x1_testbench/tb_out
VSIM 39> run -continue
VSIM 40> run -all
# time=0, in=00 sel=0 out=x
#
# time=2, in=00 sel=0 out=0
#
# time=150, in=01 sel=0 out=0
#
# time=152, in=01 sel=0 out=1
#
# time=200, in=10 sel=0 out=1
#
# time=202, in=10 sel=0 out=0
#
# time=250, in=00 sel=1 out=0
#
# time=300, in=01 sel=1 out=0
#
# time=350, in=10 sel=1 out=0
#
# time=352, in=10 sel=1 out=1
#
VSIM 41> ]

```


The 2-to-1 mux choose one of the two value based on the select value 0 or 1.

## 2. Dataflow level

### a. RTL schematic

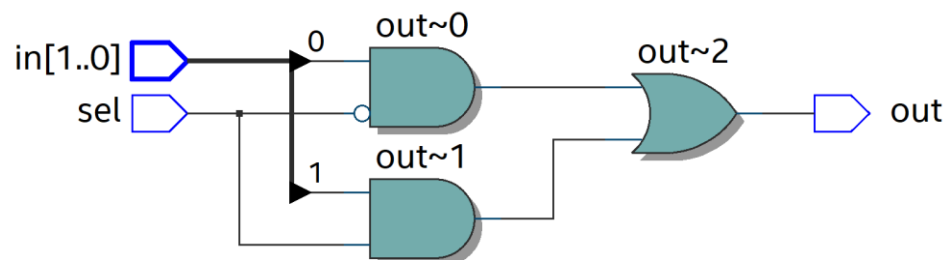

### b. Post mapping schematic

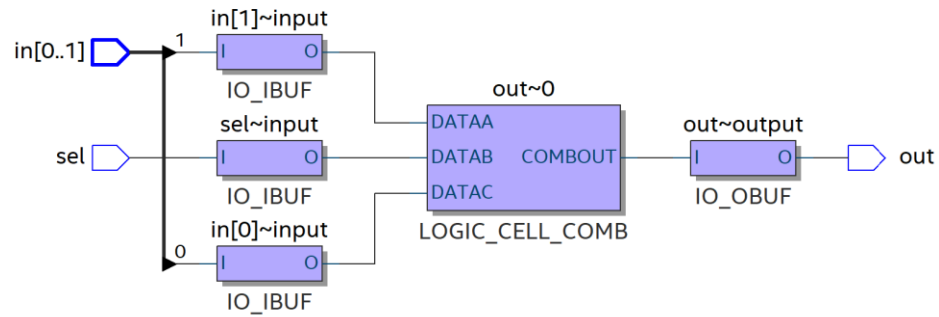


c. Resource usage

Analysis & Synthesis Resource Usage Summary		
<<Filter>>		
	Resource	Usage
1	Estimate of Logic utilization (ALMs needed)	1
2		
3	▼ Combinational ALUT usage for logic	1
1	-- 7 input functions	0
2	-- 6 input functions	0
3	-- 5 input functions	0
4	-- 4 input functions	0
5	-- <=3 input functions	1
4		
5	Dedicated logic registers	0
6		
7	I/O pins	4
8		
9	Total DSP Blocks	0
10		
11	Maximum fan-out node	out~0
12	Maximum fan-out	1
13	Total fan-out	8
14	Average fan-out	0.89


d. Modelsim simulation result (same as behavioral level simulation result)

3. Gatelevel

a. RTL schematic

 

#### b. Post mapping schematic

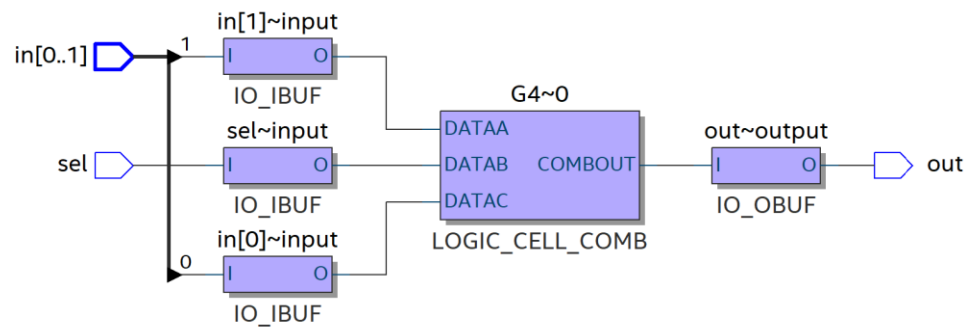

#### c. Resource usage

##### Analysis & Synthesis Resource Usage Summary

<<Filter>>


	Resource	Usage
1	Total fan-out	8
2	Total DSP Blocks	0
3	Maximum fan-out node	G4~0
4	Maximum fan-out	1
5	I/O pins	4
6	Estimate of Logic utilization (ALMs needed)	1
7	Dedicated logic registers	0
8	Combinational ALUT usage for logic	1
1	-- 4 input functions	0
2	-- 5 input functions	0
3	-- 6 input functions	0
4	-- 7 input functions	0
5	-- <=3 input functions	1
9	Average fan-out	0.89
10		
11		
12		
13		
14		

d. Modelsim simulation result (same as behavioral level simulation result)


## Full Adder

### 1. Behavioral level

#### a. RTL schematic

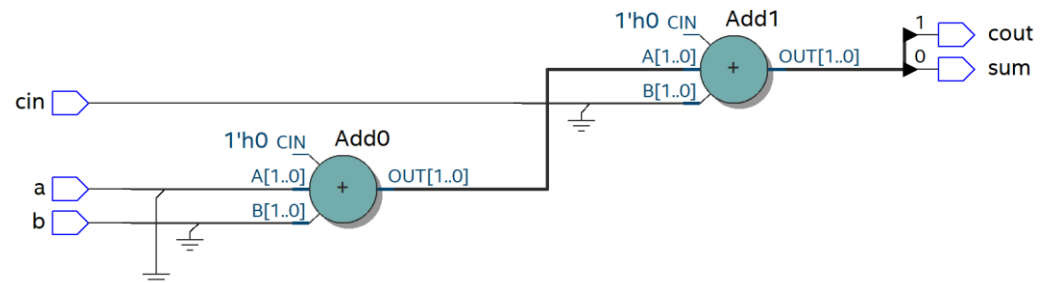

#### b. Post mapping schematic

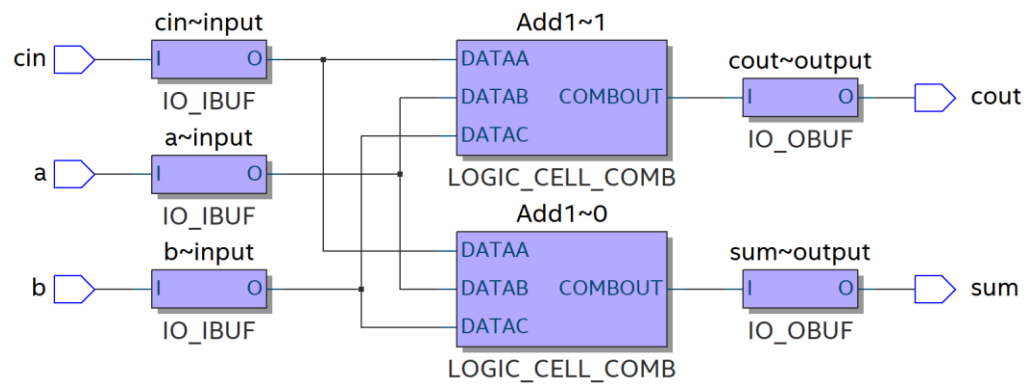

#### c. Resource usage

Analysis & Synthesis Resource Usage Summary		
<<Filter>>		
	Resource	Usage
1	Estimate of Logic utilization (ALMs needed)	1
2		
3	▼ Combinational ALUT usage for logic	2
1	-- 7 input functions	0
2	-- 6 input functions	0
3	-- 5 input functions	0
4	-- 4 input functions	0
5	-- <=3 input functions	2
4		
5	Dedicated logic registers	0
6		
7	I/O pins	5
8		
9	Total DSP Blocks	0
10		
11	Maximum fan-out node	cin~input
12	Maximum fan-out	2
13	Total fan-out	13
14	Average fan-out	1.08


**Number of ALUT: 2 (5 I/O pins)**

Full adder design need two ALUT for adding with 3 input and 2 output pins.

**Number of Functions: 2 (3 input function)**

Each output depends on all three inputs, thus 2 functions with 3 inputs

#### d. Modelsim simulation result

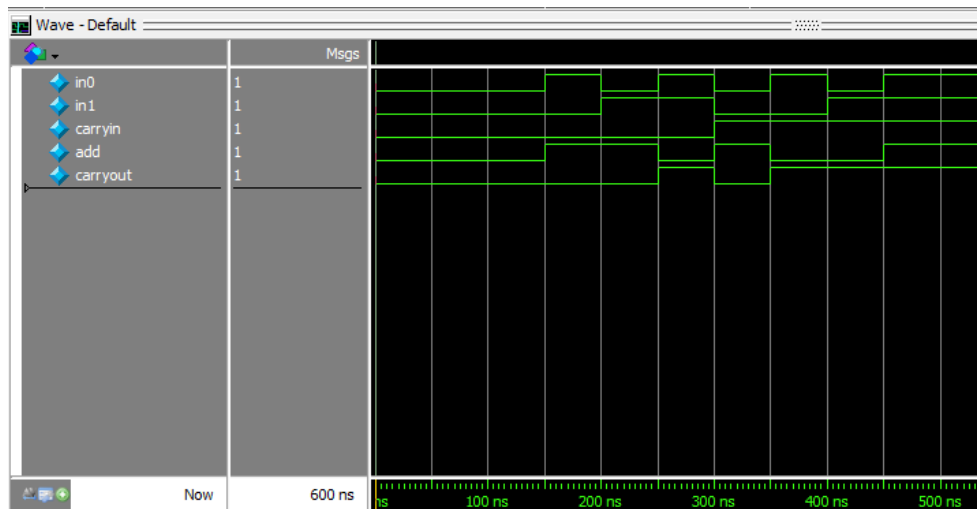

```


Transcript
# Errors: 0, warnings: 2
# vsim -gui work.fulladder_testbench
# Start time: 21:16:52 on Jul 14, 2025
# Loading sv_std.std
# Loading work.fulladder_testbench
# Loading work.fulladder
add wave -position end sim:/fulladder_testbench/in0
add wave -position end sim:/fulladder_testbench/in1
add wave -position end sim:/fulladder_testbench/carryin
add wave -position end sim:/fulladder_testbench/add
add wave -position end sim:/fulladder_testbench/carryout
VSI48> run -all
# time=0    a=0    b=0    c=0    sum=0    cout=0
#
# time=150   a=1    b=0    c=0    sum=1    cout=0
#
# time=200   a=0    b=1    c=0    sum=1    cout=0
#
# time=250   a=1    b=1    c=0    sum=0    cout=1
#
# time=300   a=0    b=0    c=1    sum=1    cout=0
#
# time=350   a=1    b=0    c=1    sum=0    cout=1
#
# time=400   a=0    b=1    c=1    sum=0    cout=1
#
# time=450   a=1    b=1    c=1    sum=1    cout=1
#

```


The full adder takes in two value with a carryin bit and return the sum for the current digit with a carryout bit if needed.

## 2. Dataflow level

### a. RTL schematic

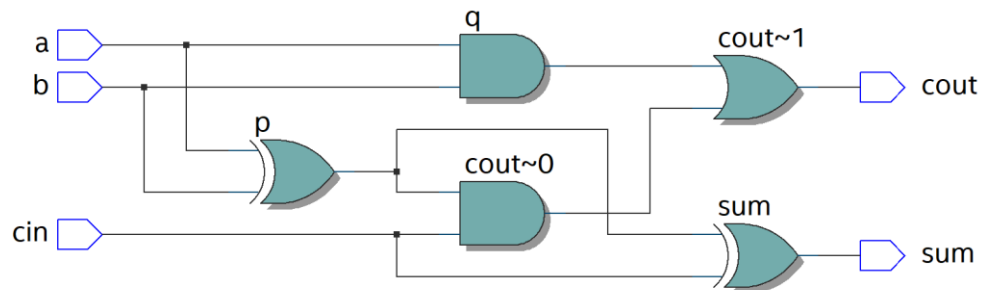

### b. Post mapping schematic

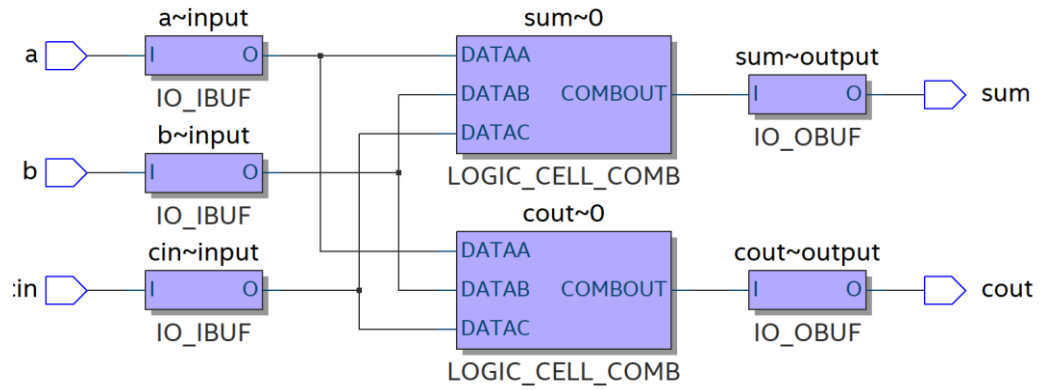

### c. Resource usage


Analysis & Synthesis Resource Usage Summary		
<<Filter>>		
	Resource	Usage
1	Estimate of Logic utilization (ALMs needed)	1
2		
3	Combinational ALUT usage for logic	2
1	-- 7 input functions	0
2	-- 6 input functions	0
3	-- 5 input functions	0
4	-- 4 input functions	0
5	-- <=3 input functions	2
4		
5	Dedicated logic registers	0
6		
7	I/O pins	5
8		
9	Total DSP Blocks	0
10		
11	Maximum fan-out node	a~input
12	Maximum fan-out	2
13	Total fan-out	13
14	Average fan-out	1.08

### d. Modelsim simulation result (same as behavioral level simulation result)


## 3. Gatelevel

### a. RTL schematic



 

**b. Post mapping schematic**

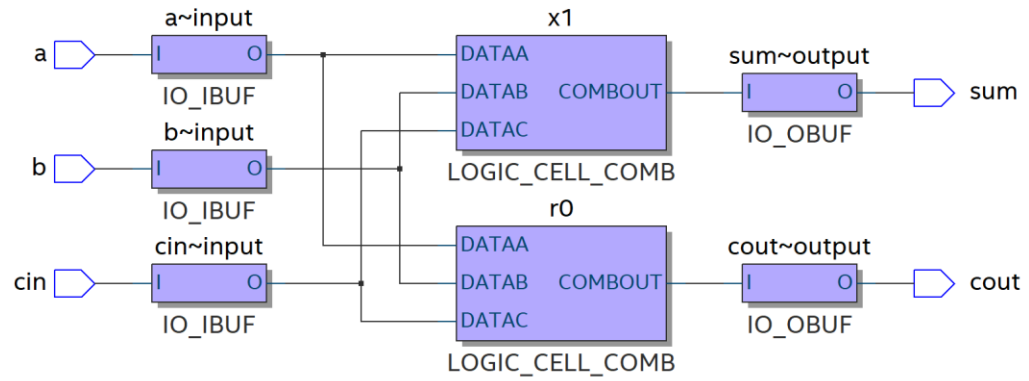

**c. Resource usage**

## Analysis & Synthesis Resource Usage Summary

 <<Filter>>

	Resource	Usage
1	Estimate of Logic utilization (ALMs needed)	1
2		
3	▼ Combinational ALUT usage for logic	2
1	-- 7 input functions	0
2	-- 6 input functions	0
3	-- 5 input functions	0
4	-- 4 input functions	0
5	-- <=3 input functions	2
4		
5	Dedicated logic registers	0
6		
7	I/O pins	5
8		
9	Total DSP Blocks	0
10		
11	Maximum fan-out node	a~input
12	Maximum fan-out	2
13	Total fan-out	13
14	Average fan-out	1.08

d. Modelsim simulation result (same as behavioral level simulation result)