

# Report HW 8 ECE-111

Name: Jasper Huang

PID: A17796149

## Handshake Synchronizer

SystemVerilog Design Code (Student added parts)

handshake\_synchronizer.sv

```
// input data register (register input data_in to data_in_reg)
always_ff@(posedge src_clk, posedge src_reset) begin
    // Student to add code here
    if (src_reset) begin
        data_in_reg <= 0;
    end else if (start && ready) begin
        data_in_reg <= data_in;
    end
end

// Data Latch :
// Control sending data from input data register through data latch
assign data = (data_out_en==1) ? data_in_reg : data;

// output data register (destination register to load data sent by sender_fsm)
always_ff@(posedge dest_clk, posedge dest_reset) begin
    if (dest_reset) begin
        data_out <= 0;
    end
    else if (data_in_en) begin
        data_out <= data;
    end
end

// Sender handshake synchronizer FSM instance
// Note : connect req_o to req_o and ack_i to sync_ack_i
sender_fsm sender_fsm_inst(
    // Student to add code here
    .src_clk(src_clk), .src_reset(src_reset),
    .start(start),
    .ready(ready),
    .data_out_en(data_out_en),
    .req_o(req_o),
    .ack_i(sync_ack_i)
);

// Receiver handshake synchronizer FSM instance
// Note : connect req_i to sync_req_i and ack_o to ack_o
receiver_fsm receiver_fsm_inst(
    // Student to add code here
    .dest_clk(dest_clk), .dest_reset(dest_reset),
    .req_i(sync_req_i),
    .ack_o(ack_o),
    .data_in_en(data_in_en)
);

// 2ff synchronizer instance for ack_o coming from receiver_fsm
// output of this synchronizer sync_ack_i will be connected to sender_fsm instance ack port
flipflop_synchronizer #(.WIDTH(1), .NUM_OF_STAGES(2)) ack_2ff_sync_inst
(
    // Student to add code here
    .clock(src_clk), .reset(src_reset),
    .d(ack_o),
    .q(sync_ack_i)
);

// 2ff synchronizer instance for req_o coming from sender_fsm
// output of this synchronizer sync_req_i will be connected to receiver_fsm instance ack_i port
flipflop_synchronizer #(.WIDTH(1), .NUM_OF_STAGES(2)) req_2ff_sync_inst
(
    // Student to add code here
    .clock(dest_clk), .reset(dest_reset),
    .d(req_o),
    .q(sync_req_i)
);
```

## sender\_fsm.sv

```
IDLE: begin
    // Student to add code here
    req_o <= 0;
    ready <= 1;
    data_out_en <= 0;
    if (start) begin
        state <= REQ_ACK_PHASE1;
    end else begin
        state <= IDLE;
    end
end

// Generate req_o = 1 to indicate handshake_rx_fsm that data is available
// Generate data_out_en = 1 to data_out_en data buffer and send data to the receiver logic
// Generate ready = 0 indicating no new req_ouest data will be accepted by tx_fm until current data is
// received by the receiver rx_fsm
// Wait for assertion of ack_i from handshake_rx_fsm
REQ_ACK_PHASE1: begin
    // Student to add code here
    req_o <= 1;
    ready <= 0;
    data_out_en <= 1;
    if (ack_i) begin
        state <= REQ_ACK_PHASE2;
    end else begin
        state <= REQ_ACK_PHASE1;
    end
end

// De-assert buffer data_out_en to 0 to latch current data until it is received by the receiver
// Continue to de-asserting of ready to 0 indicating no new data can be accepted by sender_fsm
// Wait for de-assertion of ack_i from handshake_rx_fsm
REQ_ACK_PHASE2: begin
    // Student to add code here
    req_o <= 0;
    ready <= 0;
    data_out_en <= 0;
    if (!ack_i) begin
        state <= IDLE;
    end else begin
        state <= REQ_ACK_PHASE2;
    end
end

// In Default state move to IDLE state
default: begin
    state <= IDLE;
end
```

## receiver\_fsm.sv

```
// Wait for req_iuest data coming from tx_fsm until then do not
// enable loading of data in the data register
ACK_REQ_PHASE1: begin
    // Student to add code here
    ack_o <= 0;
    data_in_en <= 0;
    state <= ACK_REQ_PHASE1;
    if (req_i) begin
        state <= ACK_REQ_PHASE2;
    end
    else begin
        state <= ACK_REQ_PHASE1;
    end
end

// In response to req_i=1 from tx_fsm, generate ack_o = 1 and enable
// loading of data in destination register and then wait for req_i = 0
ACK_REQ_PHASE2: begin
    // Student to add code here
    ack_o <= 1;
    data_in_en <= 1;
    if (!req_i) begin
        state <= ACK_REQ_PHASE1;
    end
    else begin
        state <= ACK_REQ_PHASE2;
    end
end

// In Default state move to IDLE state
default: begin
    state <= ACK_REQ_PHASE1;
end
```

## flipflop\_synchronizer.sv

```
module flipflop_synchronizer
#(parameter integer WIDTH=1, parameter integer NUM_OF_STAGES=2)
(
    input logic clock, reset,
    input logic [WIDTH-1:0] d,
    output logic [WIDTH-1:0] q
);

    logic [WIDTH-1:0] r[NUM_OF_STAGES-1:0];
    always_ff@(posedge clock, posedge reset) begin
        if(reset == 1) begin
            for(int i=0; i<NUM_OF_STAGES; i=i+1) begin
                r[i] <= 0;
            end
        end
        else begin
            r[0] <= d;
            for(int i=0; i<(NUM_OF_STAGES-1); i=i+1) begin
                r[i+1] <= r[i];
            end
        end
    end
    assign q = (reset == 0) ? r[NUM_OF_STAGES-1] : 0;
endmodule: flipflop_synchronizer
```


## Synthesis resource usage snapshot

### Analysis & Synthesis Resource Usage Summary

 <<Filter>>

|    | Resource                                    | Usage           |
|----|---------------------------------------------|-----------------|
| 1  | Estimate of Logic utilization (ALMs needed) | 38              |
| 2  |                                             |                 |
| 3  | ▼ Combinational ALUT usage for logic        | 37              |
| 1  | -- 7 input functions                        | 0               |
| 2  | -- 6 input functions                        | 0               |
| 3  | -- 5 input functions                        | 2               |
| 4  | -- 4 input functions                        | 0               |
| 5  | -- <=3 input functions                      | 35              |
| 4  |                                             |                 |
| 5  | Dedicated logic registers                   | 75              |
| 6  |                                             |                 |
| 7  | I/O pins                                    | 70              |
| 8  |                                             |                 |
| 9  | Total DSP Blocks                            | 0               |
| 10 |                                             |                 |
| 11 | Maximum fan-out node                        | src_reset~input |
| 12 | Maximum fan-out                             | 42              |
| 13 | Total fan-out                               | 504             |
| 14 | Average fan-out                             | 2.00            |

## Simulation snapshot

 

The simulation result shows the sending and receiving of four different data, where you can see for each data\_in, the cycle and their corresponding flag is output correctly with the final data\_out matching exactly as the data\_in.